

Course Number	COE328
Course Title	Digital Systems - F2022
Semester/Year	Fall 2022
Instructor	Shazzat Hossain
TA Name	Sajjad

Lab/Tutorial Report No.	Lab 2 Prelab
-------------------------	--------------

Report Title	Function Implementation and Minimization
--------------	---

Section No.	11
Group No.	N/A
Submission Date	Sept 28, 2022
Due Date	Sept 29, 2022

Student Name	Student ID	Signature*
Hamza Malik	501112545	

*By signing above you attest that you have contributed to this submission and confirm that all work you have contributed to this submission is your own work. Any suspicion of copying or plagiarism in this work will result in an investigation of Academic Misconduct and may result in a "0" on the work, an "F" in the course, or possibly more severe penalties, as well as a Disciplinary Notice on your academic record under the Student Code of Academic Conduct, which can be found online at:
<http://www.ryerson.ca/content/dam/senate/policies/pol60.pdf>

Lab 2: Function Implementation and Minimization

1 Objectives

- Implementation of simple logic functions using NAND gates
- Design, build and test logic functions using the Karnaugh map method

2 Pre-Lab Preparation

Implementation of the simple logic functions with NAND gates



- Determine 2 ways to implement an inverter with a 2-input NAND gate.
- Implement a 3-input NAND gate function using 2-input NAND gates only, draw schematics.
- Implement a 2-input OR function using 2-input NAND gates only, draw schematics.
- (A) Implement the function $Z = f(A, B) = (A + B)\bar{AB}$ using one 2-input OR gate, one 2-input AND gate and one 2-input NAND gate.
 (B) Implement the same function Z with only NAND gates.
 (C) Make up the truth table for the function. What is the common name of this function?
 (D) Expand and simplify the Boolean equation to express Z as a sum of products. Implement the sum of products using only NAND gates. Note: It is possible to do so with 4 NAND gates and no additional inverters.

PreLab:

1. Determine 2 ways to implement an inverter with a 2-input NAND gate.


Nand Gate:

x_1	x_2	F	\bar{F}
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0

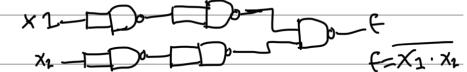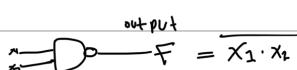


2. Implement a 3-input NAND gate function using 2-input NAND gates only, draw schematics.

Schematic: A, B

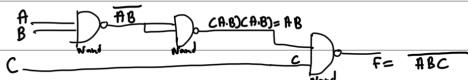


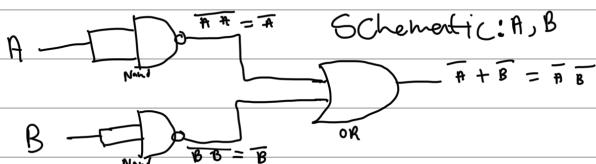3. Implement a 2-input OR function using 2-input NAND gates only, draw schematics.




4. (A) Implement the function $Z = f(A, B) = (A + B)AB$ using one 2-input OR gate, one 2-input AND gate and one 2-input NAND gate.

Schematic: A, B

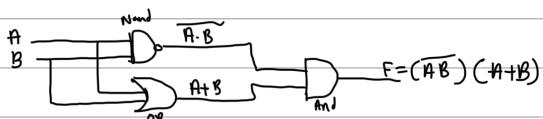

(B) Implement the same function Z with only NAND gates.

Schematic: A, B

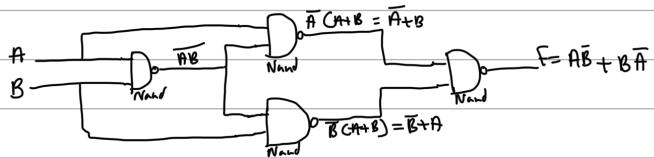

$$x + \bar{x}y = x + y$$

$$\bar{x} + xy = \bar{x} + y$$

(C) Make up the truth table for the function. What is the common name of this function?

A	B	Z
0	0	0
0	1	1
1	0	1
1	1	1

Common name of this function
is called OR function

(D) Expand and simplify the Boolean equation to express Z as a sum of products. Implement the sum of products using only NAND gates. Note: It is possible to do so with 4 NAND gates and no additional inverters.

$$\begin{aligned}
 Z &= (A+B)\overline{AB} \\
 &= (A+B)(\overline{A}+\overline{B}) \\
 &= \boxed{AB + B\overline{A}}
 \end{aligned}$$

$$A \cdot \overline{A} = 0$$

$$B \cdot \overline{B} = 0$$